



ELEX 7660: Lab 1

7-Segment LED Decoder

Table of Contents

1	Modules	3
1.1	Decode2	3
1.2	Bcitid	3
1.3	Decode7	4
1.4	Schematic.....	4
1.5	Compilation Report	5

Table of Figures

Figure 1: Decode2 Waveform	3
Figure 2: Bcitid Waveform	3
Figure 3: Decode7 Waveform	4
Figure 4: Circuit schematic created by Quartus	4
Figure 5: Compilation Report	5

1 Modules

1.1 Decode2

```
// decode2.sv - ELEX 7660 - 2 to 4 decoder. Selects which digit of the 7-segment
// LED Display to enable.
// Nicholas Huttemann 2018-01-12
module decode2 ( input logic [1:0] digit,
                 output logic [3:0] ct );

always_comb
    case(digit)
        0 : ct = 4'b0001;
        1 : ct = 4'b0010;
        2 : ct = 4'b0100;
        3 : ct = 4'b1000;
    endcase
endmodule
```

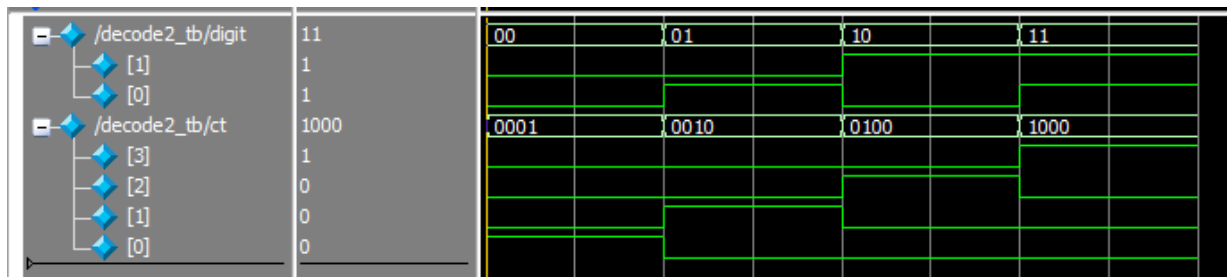


Figure 1: Decode2 Waveform

1.2 Bcidid

```
// bcidid.sv - ELEX 7660 - Module that selects and stores the last 4 digits of my
// student ID
// Nicholas Huttemann 2018-01-12
module bcidid ( input logic [1:0] digit,
                output logic [3:0] idnum );

always_comb
    case(digit)
        3 : idnum = 0;
        2 : idnum = 4;
        1 : idnum = 3;
        0 : idnum = 9;
    endcase
endmodule
```

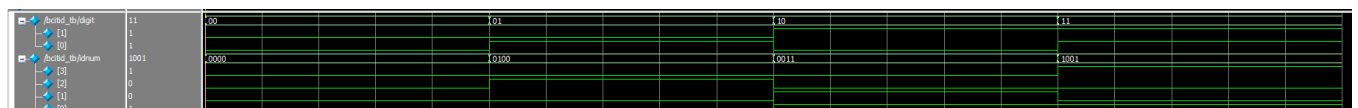


Figure 2: Bcidid Waveform

1.3 Decode7

// decode7.sv - ELEX 7660 - Converts 'num', a decimal integer 0 - 9 (10 for DP), into an 8-bit vector 'leds' that will light up corresponding segments on a 7-segment LED.

// Nicholas Huttemann 2018-01-12

```
module decode7 ( input logic [3:0] num,
                 output logic [7:0] leds);

always_comb
  case (num)
    0 : leds = 8'b11000000;
    1 : leds = 8'b111111001;
    2 : leds = 8'b10100100;
    3 : leds = 8'b10110000;
    4 : leds = 8'b10011001;
    5 : leds = 8'b10010010;
    6 : leds = 8'b10000010;
    7 : leds = 8'b11111000;
    8 : leds = 8'b10000000;
    9 : leds = 8'b10010000; //Updated to new style of 9
    10: leds = 8'b01111111;

  endcase
endmodule
```

 


Figure 3: Decode7 Waveform

1.4 Schematic

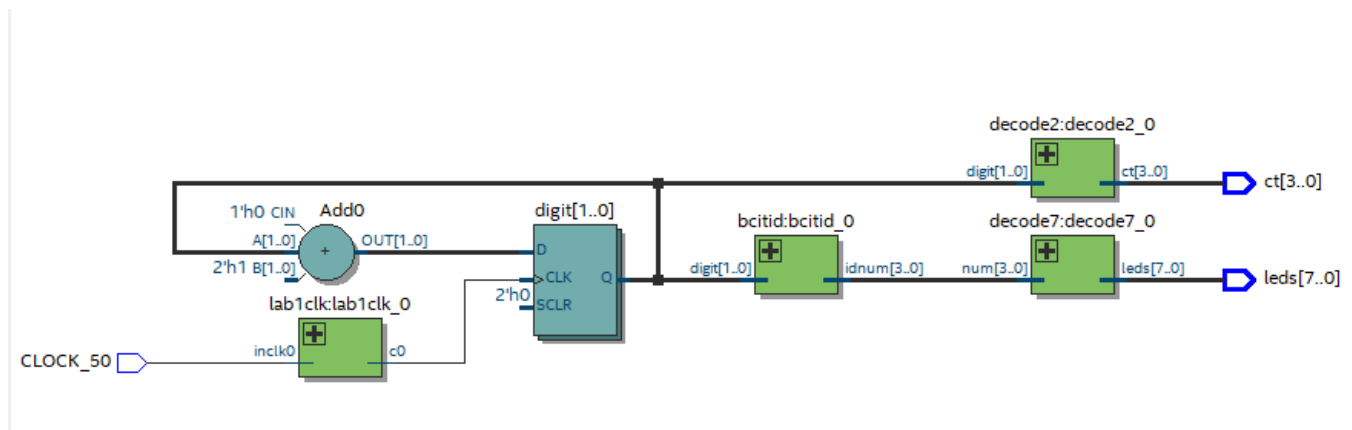


Figure 4: Circuit schematic created by Quartus

1.5 Compilation Report

Flow Status	Successful - Fri Jan 18 08:51:31 2019
Quartus Prime Version	18.0.0 Build 614 04/24/2018 SJ Lite Edition
Revision Name	Lab1
Top-level Entity Name	lab1
Family	Cyclone IV E
Device	EP4CE22F17C6
Timing Models	Final
Total logic elements	7 / 22,320 (< 1 %)
Total registers	2
Total pins	13 / 154 (8 %)
Total virtual pins	0
Total memory bits	0 / 608,256 (0 %)
Embedded Multiplier 9-bit elements	0 / 132 (0 %)
Total PLLs	1 / 4 (25 %)

Figure 5: Compilation Report